

Technical University of Cluj-Napoca

Faculty of Electronics, Telecommunications and Information Technology

2021

Computer Aided Design

Signal Generator



TECHNICAL UNIVERSITY
OF CLUJ-NAPOCA, ROMANIA

Supervisor:

SI.Dr.Ing. Raul FIZEȘAN

Student:

Diana Elena MIRCEA

Group: 2023

1 Documentation part

1.1 Requirements

Design a signal generator that provides a rectangular signal of variable amplitude {4V, 7V}, and a triangular signal of 4V amplitude. The frequency of the signal should range between [2400; 9100][Hz], the power supply has the amplitudes [-15;+15] [V] and the load resistance has a value of 10[Ω].

1.2 Block Diagram



1.2.1 Block 1: Rectangular signal generator- Positive feedback comparator

The first block represents an Op-amp multivibrator or attenuation oscillator (positive feedback comparator), which will give at the output a rectangular signal, having the amplitude equal to the saturation voltage of the power supply.

An oscillator is a circuit that uses only a dc voltage supply as input, to produce a periodic waveform on its output. A relaxation oscillator is part of a major category of oscillators, that work based on an RC timing circuit and a device that changes states.

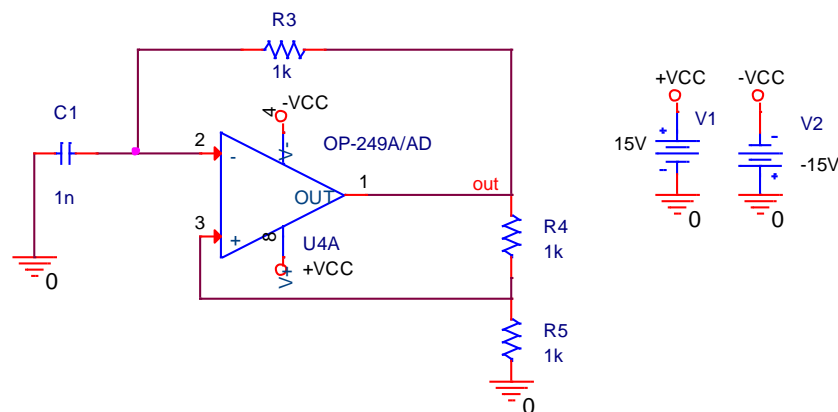


Figure 1- Astable multivibrator (Positive feedback comparator)


That device will be a positive feedback comparator- an op-amp circuit that compares two input voltages and delivers at the output its maximum or minimum saturation voltage provided, depending on the relationship between the inputs. Because the op-amp has a high open-loop voltage gain, it is very sensitive to the voltage changes on its inputs, and the output can switch

uncontrollably between its positive, $+V(\text{sat})$ and negative, $-V(\text{sat})$ supply rails whenever the input voltage being measured is near to the reference voltage, V_{REF} , as in Graph 1. In figure 1, V_{REF} is the voltage divider between R4 and R5, and it's value can be computed using formulas (1) and (2).

The RC timing network is connected to the inverting input of the operational amplifier and the voltage divider network is connected to the non-inverting input.

The Op-Amp is constantly switching between two states with the time spent in each state controlled by the charging or discharging of the capacitor through the resistor.

At the beginning, when the circuit is turned on, the capacitor is not charged, therefore the inverting output will have 0V, and the noninverting input will have a greater voltage, making the circuit to deliver a maximum voltage at the output. The capacitor begins to charge through resistance R3, until it reaches a certain voltage that is equal or greater than the voltage of the noninverting input, V_{ref} . In that moment, the op-amp will switch to its minimum value, and the capacitor will be fed with a negative voltage, making it to discharge until it reaches $-V_{\text{ref}}$. This process repeats infinitely, and a rectangular wave will be obtained at the output.

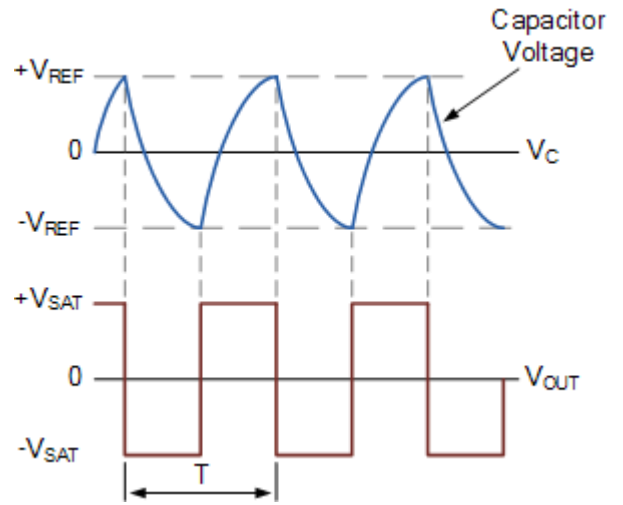

Graph 1-Voltage on the capacitor (V_c), voltage at the output (V_{out})

Formulas:

$$-V_{\text{REF}} = \frac{R5}{R4+R5} * (-V_{\text{SAT}}) \quad (1)$$

$$+V_{\text{REF}} = \frac{R5}{R4+R5} * V_{\text{SAT}} \quad (2)$$

We denote:
$$\beta = \frac{R5}{R4+R5} \quad (3)$$

Period of the signal:
$$T = 2C_1R_3 \ln \frac{1+\beta}{1-\beta} \quad (4)$$

Frequency of the signal:
$$f = \frac{1}{T} \quad (5)$$

R is Resistance, C is Capacitance, $\ln(\)$ is the Natural Logarithm, T is periodic time in seconds, and f is oscillation frequency in Hz. Formulas from above are presented in [5].

1.2.2 Block 2. Triangular waveform-Integrator-Active LowPass Filter

To obtain a triangular waveform, we can enhance the astable multivibrator circuit presented before, making the voltage on the capacitor while charging/discharging, linear. By knowing the formula for the voltage on the capacitor:

$$v_c(t) = \frac{1}{C} \int_{t_1}^{t_2} i_c dt \quad (6)$$

We can deduce that if the current through the capacitor is constant, the voltage will be a linear variation in time, which is exactly what we want to obtain:

$$v_c(t) = \frac{1}{C} I_c t \Big|_{t_1}^{t_2} \quad (7)$$

As shown above, an op-amp integrator simulates the mathematical process of integration, determining in this way the instantaneous rate of change of a function. Practical integrators often have an additional resistor or other circuitry in parallel with the feedback capacitor to prevent saturation. The circuit can be seen in figure 2.

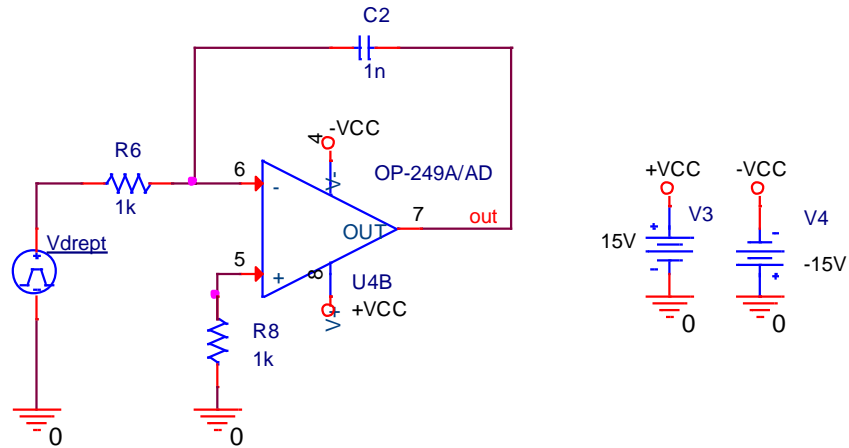


Figure 2-Integrator


Considering V_{drept} a rectangular voltage that is applied to the input of an integrating amplifier. At the beginning: the capacitor C2 is uncharged and acts as a short circuit, maximum current is drawn by the input resistance R_{in} . Since no current flows into the Op-Amp, the non-inverting input is connected to the ground, and the voltage at point 6, V^- , is equal to the voltage at point 5, V^+ ; the point 6 will be a virtual ground, resulting in zero at the output.

As the capacitor starts to slowly charge due to the influence of V_{drept} , the voltage on the negative side of the capacitor, which is also the output of the Op-Amp, decreases linearly from 0, until the capacitor is fully charged. This voltage is called negative ramp, and is a consequence of a constant positive input.

The rate of change of the output is the rate of change at which the capacitor charges, determined by the RC time constant, described by formula (8), presented in [1].

$$\frac{\Delta V_{out}}{\Delta t} = - \frac{V_{drept}}{R_6 C_2} \quad (8)$$

When it is fully charged, the capacitor acts as an open circuit, blocking any flow of DC current. The ratio of capacitor reactance to input resistance is now infinite resulting in infinite gain. The result of this high gain is that the output of the amplifier goes into saturation as shown in graph 2.

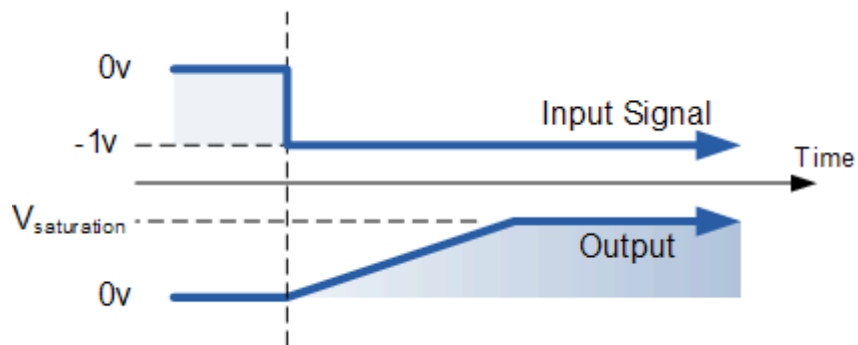

Graph 2- Output signal of an integrator in comparison with the input voltage

If we apply a constantly changing input signal such as a square wave to the input of an integrator amplifier then the capacitor will charge and discharge in response to changes in the input signal, as in graph3.


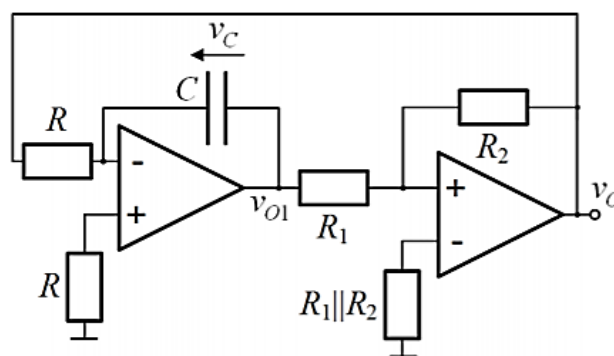


Figure 3- Integrator circuit

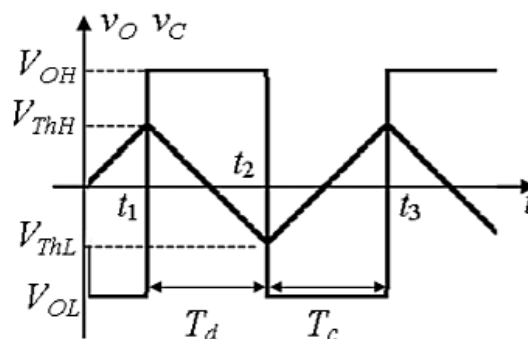

Graph 3-Output signal of an integrator, when is fed with a rectangular voltage

The output of the first amplifier in the picture above, which is also the voltage on the capacitance, V_{O1} , will have the amplitude equal to:

$$V_{ThL} = -\frac{R1}{R2}V_{OH} \quad (9)$$

$$V_{ThH} = -\frac{R1}{R2}V_{OL} \quad (10)$$

Discharge time: $T_d = RC \frac{V_{ThH} - V_{ThL}}{V_{OH}} \quad (11)$

Charge time: $T_c = RC \frac{V_{ThH} - V_{ThL}}{-V_{OL}} \quad (12)$

In general : $V_{OH} = -V_{OL}$

Period of a triangle wave: $T = T_c + T_d = 2RC \frac{V_{ThH} - V_{ThL}}{V_{OH}} \quad (13)$

1.2.3 Block 3 -Frequency Adjuster

In order to adjust the frequency of the oscillator, we have to change the time constant of the circuit, which means to change either the capacitor value, either the resistance. I plan to use a structure based on a potentiometer and a resistor, seen by the resistance on the inverting input of the integrator. The full circuit at this stage should look like in figure 4.

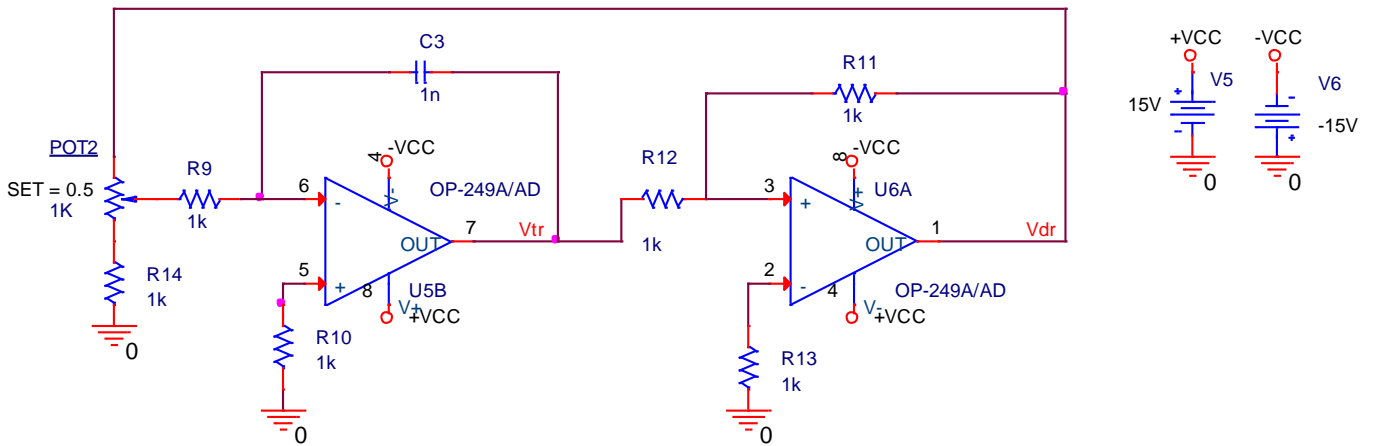


Figure 4-Triangle signal generator with adjustable frequency

In this way, we can compute the frequency range of the circuit, using the formulas presented in [5].

$$f_{\max} = \frac{1}{4R_9C_3} \frac{R_{11}}{R_{12}} \quad (14)$$

$$f_{\min} = \frac{1}{4R_9C_3} \cdot \frac{R_{11}}{R_{12}} \cdot \frac{R_{14}}{R_{14} + \text{POT}_2} \quad (15)$$

1.2.4 Block 4-Amplitude adjustment

The amplitude of the rectangular wave at the output of the positive comparator is approximately 15V. Therefore, we need to adjust this voltage to either 4 V, or 7V.

I plan to do this by using a structure based on a potentiometer, two resistors, and a voltage follower to match the impedances of the resistors to the load.

The gain of the Op-Amp is 1, and the voltage of the noninverting input is going to be the same as the voltage at the output, it does not affect the signal's amplitude.

In this circuit, in order to obtain the desired amplitude of the signal, the resistances used have a smaller impedance compared to the one of the load, and this may cause impedance mismatching. The usefulness of the buffer comes from that it's input impedance is really high, while the impedance at the output is low, solving the impedance problem.

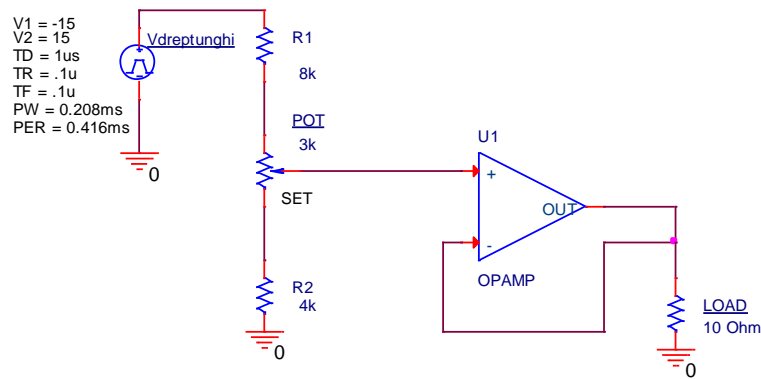


Figure 5-Amplitude adjuster

The formulas for the output voltage, depending on the position of the potentiometer:

$$\text{Set}=0: \quad V_{out_{min}} = \frac{R2}{R1+POT+R2} * V_{drept} \quad (16)$$

$$\text{Set}=1: \quad V_{out_{max}} = \frac{POT+R2}{R1+POT+R2} * V_{drept} \quad (17)$$

1.2.5 Block5- power amplifier

The current at the output of the Op-Amp should be about 400mA when the output voltage is 4V and about 700mA when the output voltage is 7V. But because a the UA741 opAmp can't provide such a big current, I used a Class AB power amplifier with a shortcircuit protection for higher currents.

The amplifier works like this: on the positive half of the input signal, the npn transistor T_n is in conduction, and it uses 0.7V from the input signal V_I , for its V_{BE} , base to emitter voltage. To make the output signal to get back the 0.7V lost on the transistor T_n , I placed a diode D_1 that will provide the biasing voltage to this part of the circuit. T_p and D_2 work for the negative half of the input voltage V_I , symmetrically.

The current in the diodes and transistors are the same, building a current mirror that eliminates the crossover distortion appeared in class B amplifier. To prevent a higher current flow through the diodes, resistors R are added to alleviate the thermal runaway.

Using the formulas from [1], the diode current is the same as I_{CQ} , the collector current in the transistor T_n :

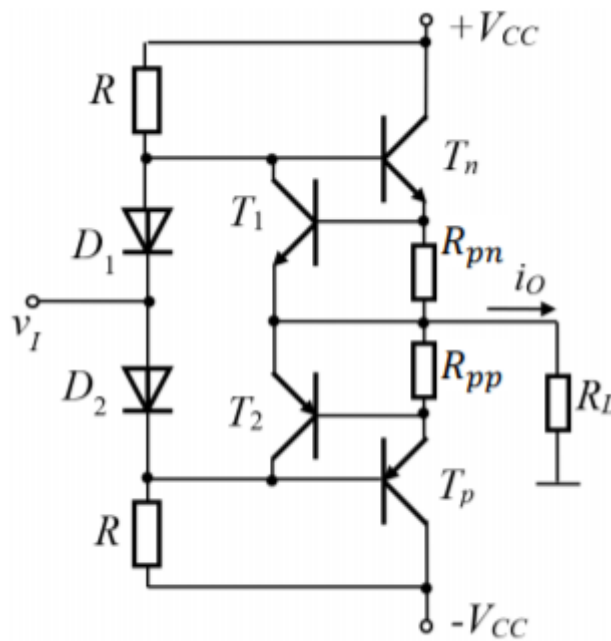


Figure 6-Class AB power amplifier

$$I_{CQ} = \frac{V_{CC} - 0.7V}{R} \quad (18)$$

The ideal maximum peak output voltage is

$$V_{outPeak} = V_{CEQ} = V_{CC} = 15V \quad (19)$$

The ideal maximum peak current is:

$$I_{outPeak} = I_{Csat} = \frac{V_{CC}}{R_L} = \frac{15}{10} = 1.5A \quad (20)$$

The elements responsible for the short-circuit protection are: **T1,T2, Rpn, Rpp**.

When the output voltage V_o is positive and the voltage drop on the resistance R_{pn} is $R_{pn} * I_o < 0.7V$, then T1 is off and I_o is given by the formulas from [9] :

$$I_o = \frac{V_o}{R_L} \quad (20)$$

When I_o increases, and when the voltage drop $R_{pn} * I_o = 0.7V$, then T1 will enter conduction and

$$I_{o\max} = \frac{V_{BE}}{R_{pn}} = \frac{0.7V}{R_{pn}} \quad (21)$$

To compute the resistances R from fig 6, I used formulas from [10]:

$$V_{CC} = 2 * R * I_{bias} + 2 * V_{BE}$$

$$R = \frac{V_{CC} - 2 * V_{BE}}{2 * I_{bias}}$$

$$I_{bias} = 0.02 * I_{Csat} = 0.02 * \frac{V_{CC}}{2R_L}$$

The testing block from ORCAD: The amplifier magnifies the output current of the OpAmp

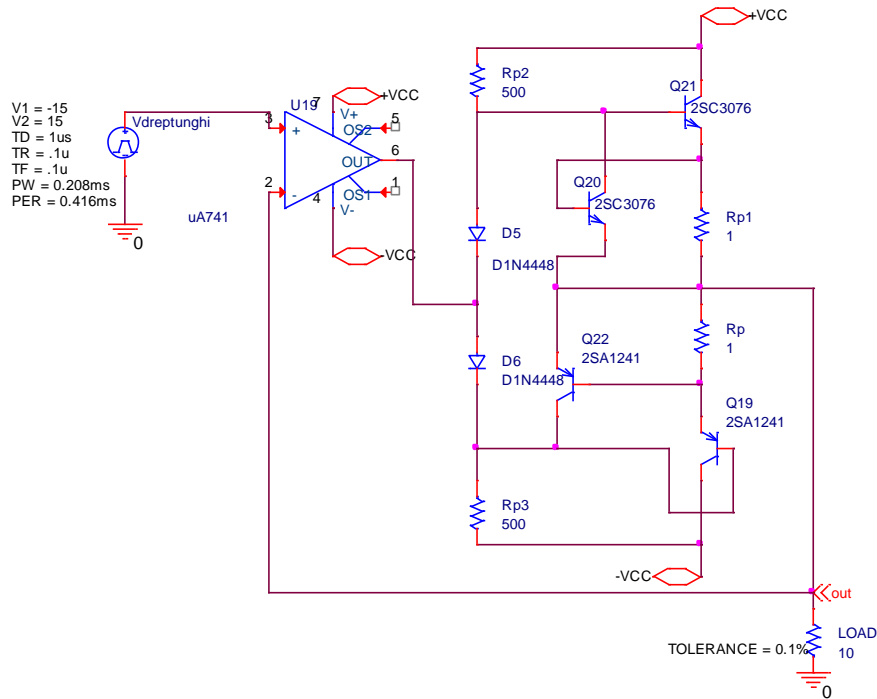


Figure 7-Class AB Power Amplifier - ORCAD

2 The final circuit

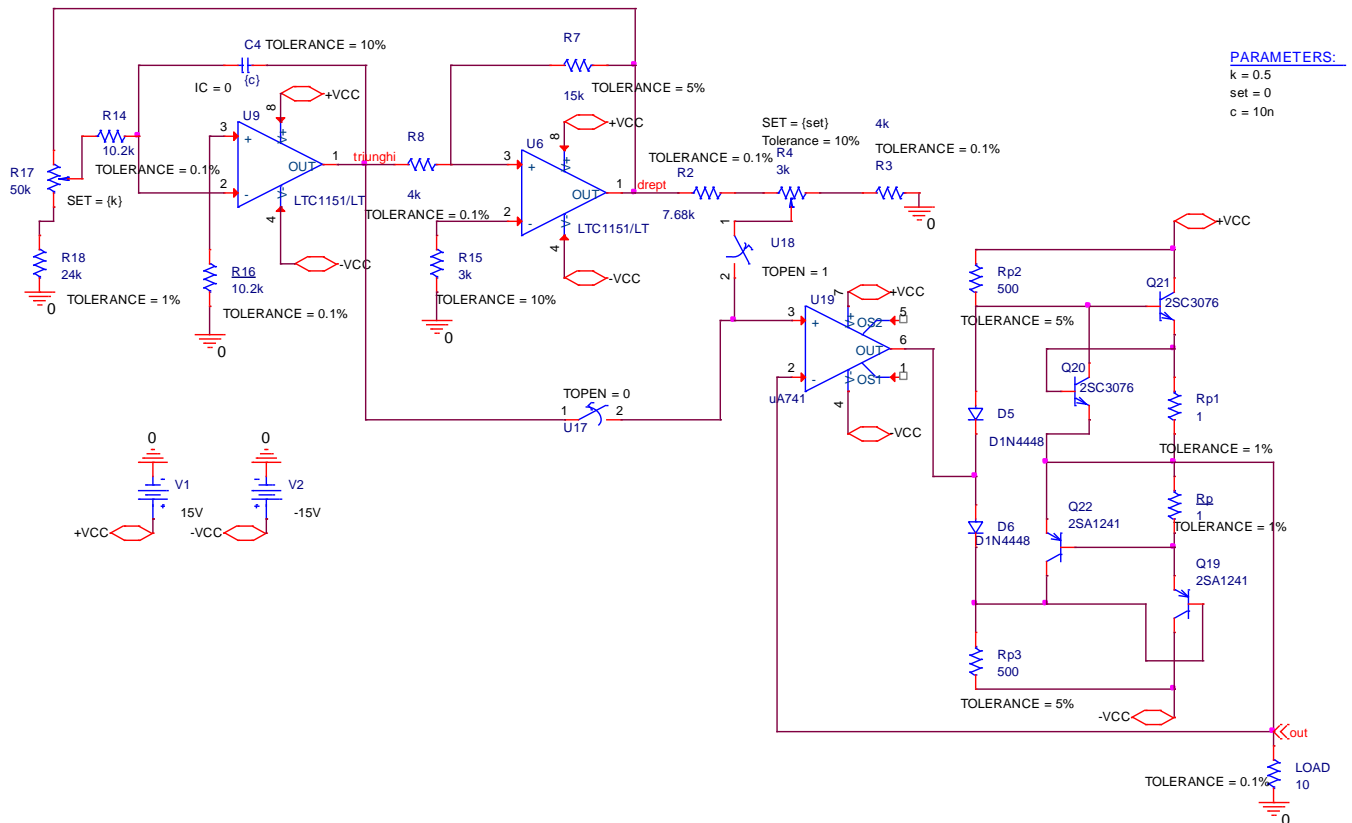


Figure 8-FINAL CIRCUIT-ORCAD

3 Calculus

Compute the amplitude of the triangle wave:

$$V_{triunghi} = \frac{R8}{R7} V_{OH} = \frac{R8}{R7} 15 = 4 \text{ V} \quad \Rightarrow \text{R7}=15\text{k}\Omega; \text{R8}=4\text{k}\Omega$$

R15=R8||R7=3kΩ (for stabilizing the opamp)

Compute the amplitude of the rectangular wave:

$V_{load}(\text{rectangle})$ has to be either **4V** or **7 V**
 Set=0: $V_{load_{min}} = \frac{R3}{R2+R4+R3} * 15 = 4V$

Set=1: $V_{load_{max}} = \frac{R_4+R_3}{R_2+R_4+R_3} * 15=7V$

$$R2 + R4 + R3 = \frac{R3 * 15}{4} = \frac{(R4 + R3) * 15}{7}$$

$$7R3=4R4+4R3 \Rightarrow 3R3=4R4 \Rightarrow \mathbf{R3=4k\Omega ; R4=3k\Omega}$$

$$R2 + R4 + R3 = \frac{4k*15}{4} = 15k = R2 + 3k + 4k \Rightarrow \mathbf{R2 = 15k - 7k = 8k\Omega}$$

Compute the frequency of the signal:

$$f_{\max} = \frac{1}{4R_{14}C_4} \frac{R_7}{R_8} = \frac{1}{4R_{14}C_4} \frac{15k}{4k} = 9100 \text{ Hz} \Rightarrow R_{14} * C_4 = \frac{15}{4*9100} = 103 \text{ u} \Rightarrow$$

$$\mathbf{R_{14} = 10.3k\Omega; C_4 = 10nF}$$

R16=R14=10.3kΩ (for stabilizing the opamp)

$$f_{\min} = \frac{1}{4R_{14}C_4} \frac{R_7}{R_8} \cdot \frac{R_{18}}{R_{18}+R_{17}} = 2400 \text{ Hz} \Rightarrow \frac{R_{18}}{R_{18}+R_{17}} = \frac{2400}{9100} \Rightarrow$$

$$91R_{18} = 24R_{18} + 24R_{17} \Rightarrow 67R_{18} = 24R_{17} \Rightarrow \mathbf{R_{18} = 24k\Omega; R_{17} = 67k\Omega}$$

Sizing the elements of the power amplifier:

The OpAmp U19 used is an **uA741**. The diodes D5 and D6 are fast switching diodes **D1N448**

Using the formulas (21) we can compute the protection resistances Rpn, Rpp from fig6:

$$R_{pn} = R_{pp} = \frac{0.7V}{I_{o\max}} \quad \text{If we choose the maxim output current } 0.8A$$

$$\mathbf{R_{pn} = R_{pp} = \frac{0.7V}{0.8A} \sim 1\Omega}$$

To compute the resistances R from fig 6:

$$I_{bias} = 0.02 * I_{Csat} = 0.02 * \frac{V_{CC}}{2R_L} = 0.02 * \frac{15}{2 * 10} = 15mA$$

$$\mathbf{R = \frac{15 - 2 * 0.7}{2 * 0.015} = 453 \sim 450\Omega}$$

As for the transistors, I used **2SC3076** for the NPN and **2SA1241** for the PNP, because the maximum collector current $I_C=2A$, which is greater than $1.5A$ ($I_{outPeak}$).

2SC3076

POWER AMPLIFIER APPLICATIONS

POWER SWITCHING APPLICATIONS

- Low Collector Saturation Voltage
: $V_{CE(sat)} = 0.5 \text{ V (Max.)}$ ($I_C = 1 \text{ A}$)
- Excellent Switching Time : $t_{stg} = 1.0 \mu\text{s}$ (Typ.)
- Complementary to 2SA1241

MAXIMUM RATINGS ($T_a = 25^\circ\text{C}$)

CHARACTERISTIC	SYMBOL	RATING	UNIT
Collector-Base Voltage	V_{CBO}	50	V
Collector-Emitter Voltage	V_{CEO}	50	V
Emitter-Base Voltage	V_{EBO}	5	V
Collector Current	I_C	2	A
Base Current	I_B	1	A
Collector Power Dissipation	P_C	1.0	W
		10	
Junction Temperature	T_j	150	$^\circ\text{C}$
Storage Temperature Range	T_{stg}	$-55 \sim 150$	$^\circ\text{C}$

Unit in mm

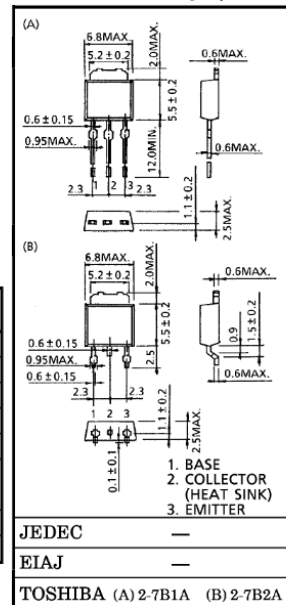


Figure 9 -Datasheet of the NPN transistor

For the block that give rectangular and triangular waveforms, I used an operational amplifier **LTC1151/LT** which gives an output voltage swing of $\pm 14.99\text{V}$

List of real components:

Component	Theoretical value	Real value	Tolerance	From where to buy	Price
Resistor	24k Ω	24k Ω	+/-1%	https://ro.farnell.com/multicomponent/mf25-24k/res-24k-1-250mw-axial-metal-film/dp/9341609	0.19lei/pcs Min 10pcs
Resistor	10.3k Ω	10.2k	+/-0.1%	https://ro.farnell.com/te-connectivity/rp73pf1j10k2btdf/res-10k2-0-1-0-166w-0603-thin/dp/2116785	2.71lei/1pcs
Resistor	4k Ω	4k	+/-0.1%	https://ro.farnell.com/multicomponent/mcknp03uj0402b00/wirewound-resistor-4kohm-3w-5/dp/1602143	4.31lei/pcs x2=8.62lei
Resistor	15k Ω	15k	+/-5%	https://ro.farnell.com/w/c/passive-components/resistors-fixed-value/prl/rezultate?resistance=15kohm&packaging=each	0.65lei/pcs
Resistor	3k Ω	3k	+/-5%	https://ro.farnell.com/multicomponent/mcknp03uj0302b00/res-3k-5-3w-axial-wirewound/dp/1903845	3.14lei/pcs
Resistor	8k Ω	7.68k	+/-0.1%	https://ro.farnell.com/neohm-te-connectivity/yr1b7k68cc/res-7k68-0-10-250mw-axial/dp/1083350	3.18lei/pcs
Resistor	10 Ω	10	+0.1%	https://ro.farnell.com/neohm-te-connectivity/yr1b10rcc/res-10r-0-10-250mw-axial/dp/1083036	3.39lei/pcs
Resistor	500 Ω	500	+/-5%	https://ro.farnell.com/multicomponent/mcknp01wj0501a10/res-500r-5-1w-axial-wirewound/dp/1903699	0.91lei/pcs x2=1.82lei
Resistor	1 Ω	1	+/-1%	https://ro.farnell.com/vishay/mbb02070c1008fc100/res-1r-1-600mw-axial-thin-film/dp/2614375	0.59lei/pcs x2=1.2lei
Potentiometer	67k Ω	50k	+/-20%	https://ro.farnell.com/bourns/3310p-001-503l/potentiometer-50k/dp/1156136	12.75lei/pcs
Potentiometer	3k Ω	3k Single turn	+/-10%	https://ro.farnell.com/bourns/3362p-1-302lf/trimmer-pot-3kohm-10-1turn-th/dp/2328607	5.35lei/pcs
Capacitor	10nF	0.01uF	+/-10%	https://ro.farnell.com/vishay/mkt1813310635g/cap-0-01-f-630v-10-pet/dp/1166871	13.85lei/pcs

OpAmp	Model: LTC1151			https://www.ebay.com/p/661301885	53.94lei/pcs X2=108lei
OpAmp	UA741ID			https://ro.farnell.com/stmicroelectronics/ua741id/op-amp-single-1mhz-0-5v-s-8/dp/1842613?st=ua741	18.5lei/pcs
Diode	1N4148TA			https://ro.farnell.com/on-semiconductor/1n4148ta/diode-ultrafast-300ma-100v-do/dp/2322485?st=1n4148	0.73lei/pcs x5=3.65lei
Transistor	2SC3076			https://store.americanmicrosemiconductor.com/2sc3076y.html?mcid=7	2.34lei/pcs x2=4.68lei
Transistor	2SA1241			https://www.utsource.net/itm/p/752906.html?digipart=1	3.52lei/pcs x2=7.04lei

4 Analyzes

a. Transient Analysis

➤ The Triangle of 4V

Frequency:

- for the potentiometer **R17** with **k=0.5**

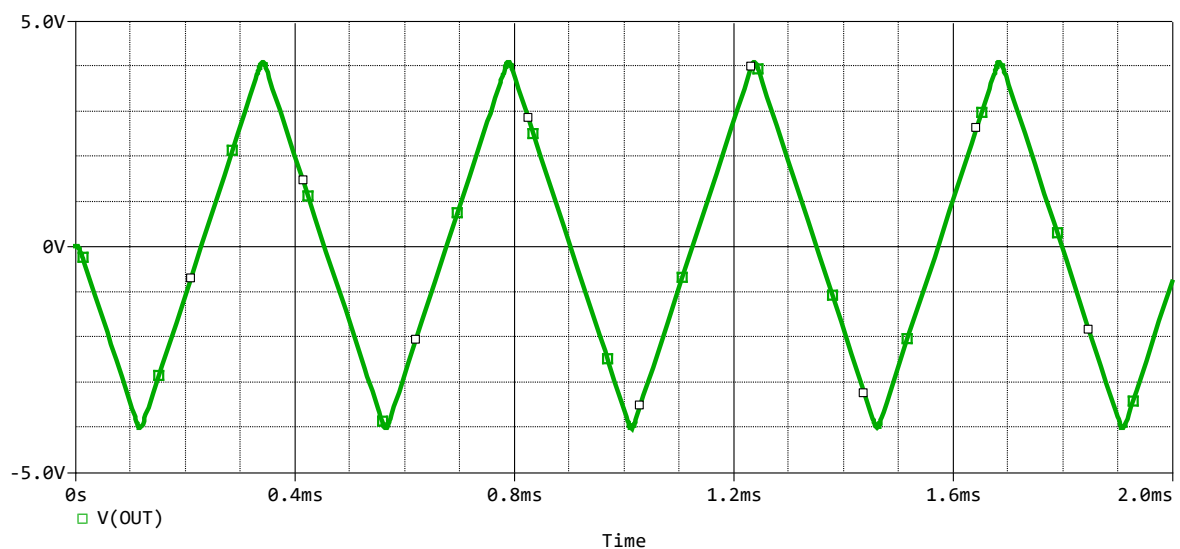


Figure 10-Triangle wave-frequency of 2237Hz

Evaluate	Measurement	Value
<input checked="" type="checkbox"/>	Period(V(triunghi))	447.92366u
<input checked="" type="checkbox"/>	Period(V(load:2))	447.92350u

$$f = \frac{1}{T} = \frac{1}{447u} = 2237Hz$$

- for the potentiometer **R17 with k=0**

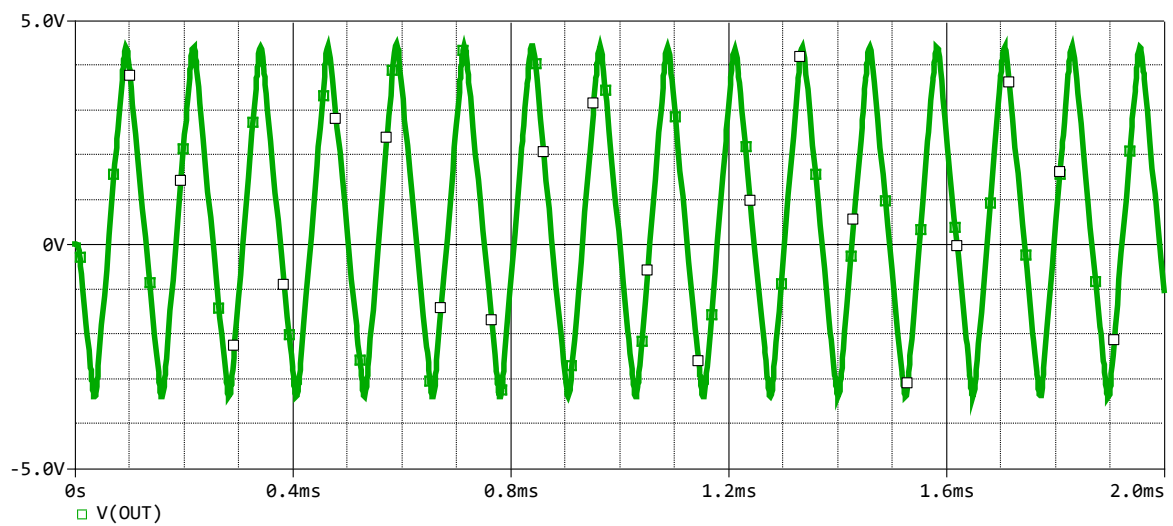


Figure 11-Triangle wave-frequency of 8130

Evaluate	Measurement	Value
<input checked="" type="checkbox"/>	Period(V(triunghi))	123.44171u
<input checked="" type="checkbox"/>	Period(V(load:2))	123.44088u

$$f = \frac{1}{T} = \frac{1}{123u} = 8130Hz$$

➤ The Rectangle

The setting **Set=0** will ensure an amplitude of 4V

Frequency:

- for the potentiometer **R17 with k=0**

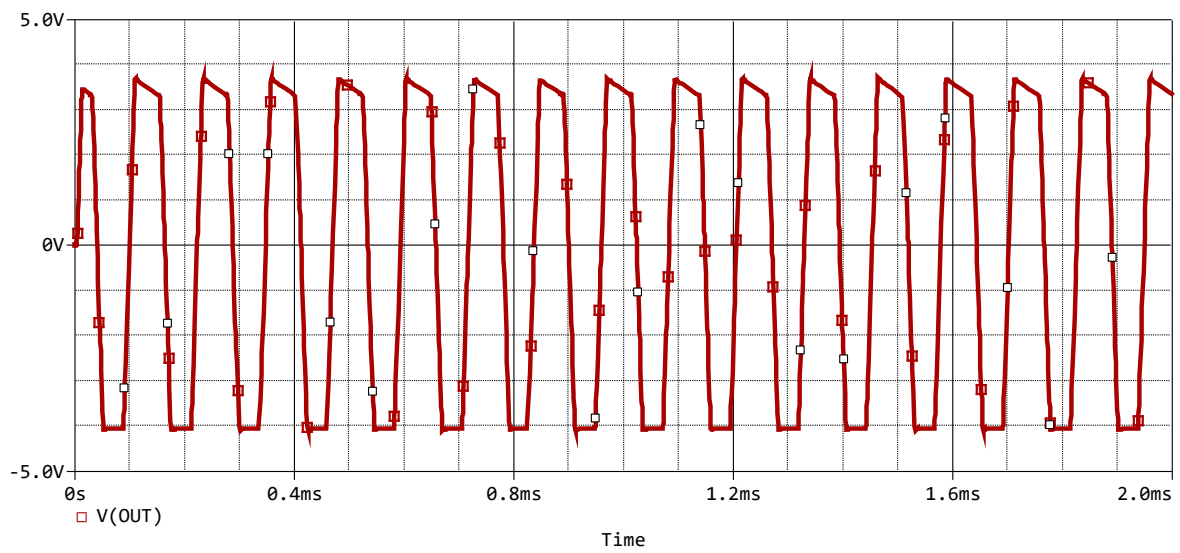


Figure 12-Rectangular-4V-frequency 8130Hz

Evaluate	Measurement	Value
<input checked="" type="checkbox"/>	Period(V(drept))	123.53691u
<input type="checkbox"/>	Period(V(triunghi))	
<input checked="" type="checkbox"/>	Period(V(load:2))	123.55814u

- for the potentiometer **R17** with **k=0.5**

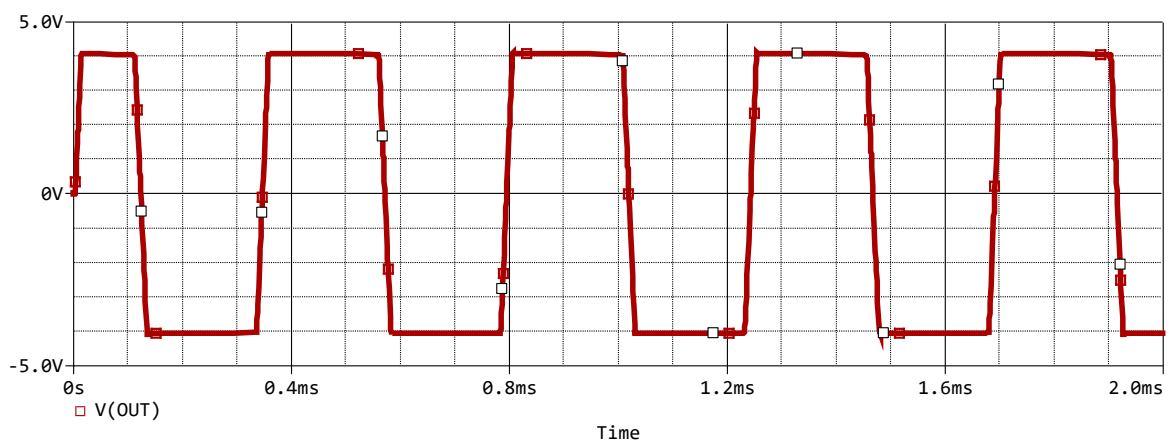


Figure 13-Rectangular-4V-frequency 2237Hz

Evaluate	Measurement	Value
<input checked="" type="checkbox"/>	Period(V(drept))	339.67462u
<input type="checkbox"/>	Period(V(triunghi))	
<input checked="" type="checkbox"/>	Period(V(load:2))	448.04571u

The setting **Set=1** will ensure an amplitude of 7V

- for the potentiometer **R17 with k=0.5**

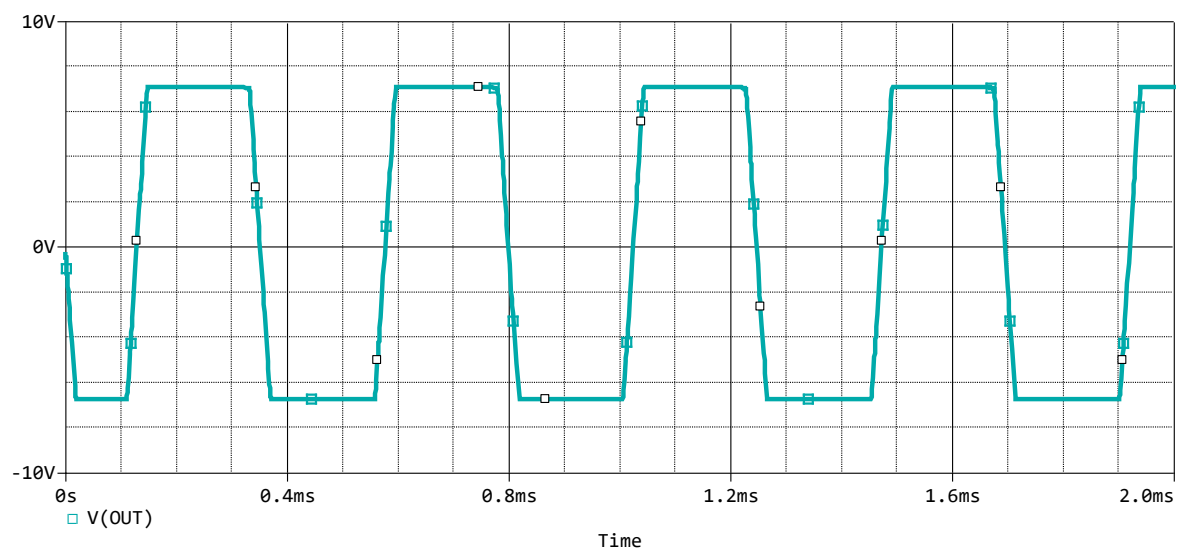


Figure 14-Rectangular-7V-frequency 2237Hz

Evaluate	Measurement	Value
<input type="checkbox"/>	Period(V(triunghi))	
<input checked="" type="checkbox"/>	Period(V(load:2))	447.79941u
<input checked="" type="checkbox"/>	Max(V(out))	7.09081

- for the potentiometer **R17 with k=0**


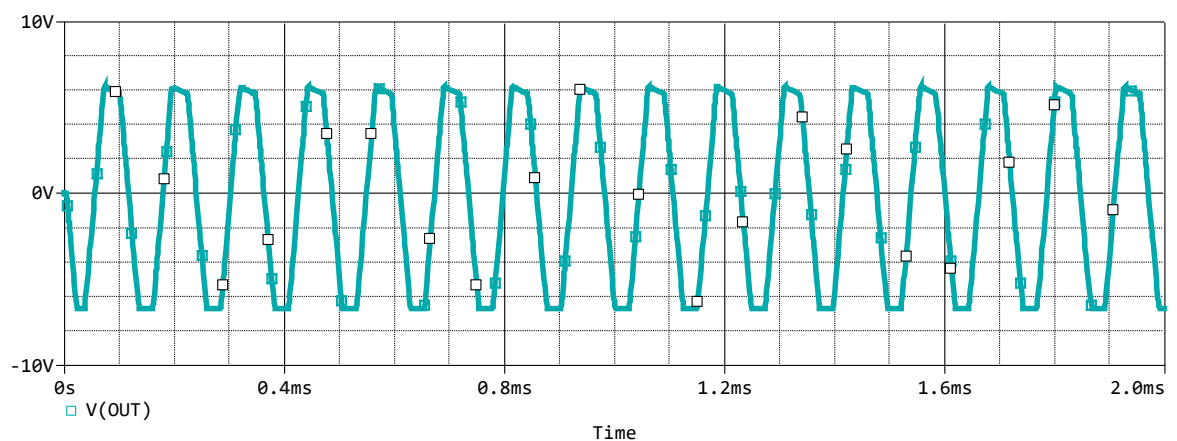


Figure 15-Rectangular-6.21V-frequency 8130Hz


Evaluate	Measurement	Value
<input checked="" type="checkbox"/>	Period(V(load:2))	123.80873u
<input checked="" type="checkbox"/>	Max(V(out))	6.21063

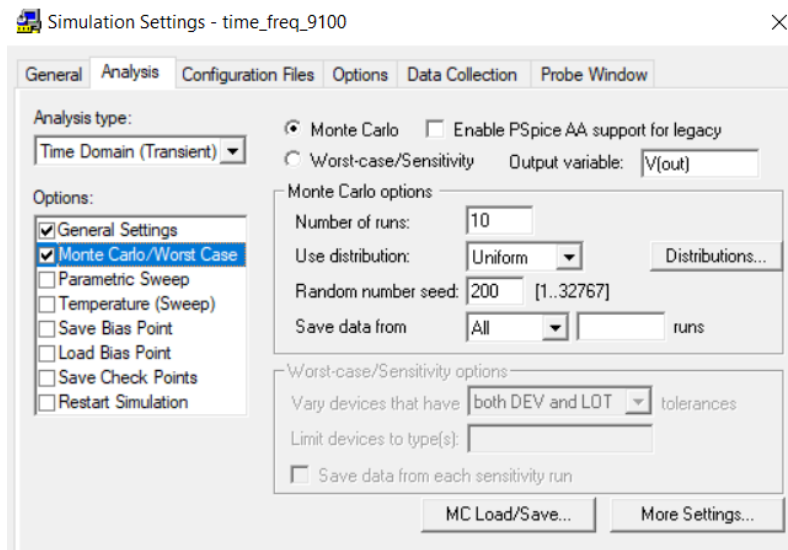b. Sensitivity Analysis


Results of running a **Monte Carlo Analysis** to test the **tolerances of the components**:



Simulation setting 1- Monte Carlo

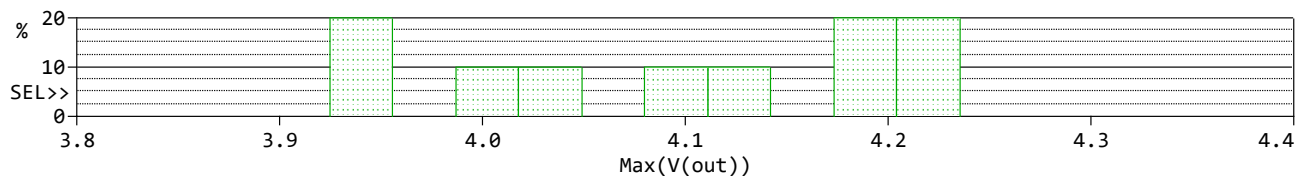


n samples	= 10	sigma	= 0.112986	median	= 4.11577	3*sigma	= 0.338957
n divisions	= 10	minimum	= 3.92459	90th %ile	= 4.2217		
mean	= 4.09758	10th %ile	= 3.93449	maximum	= 4.23527		

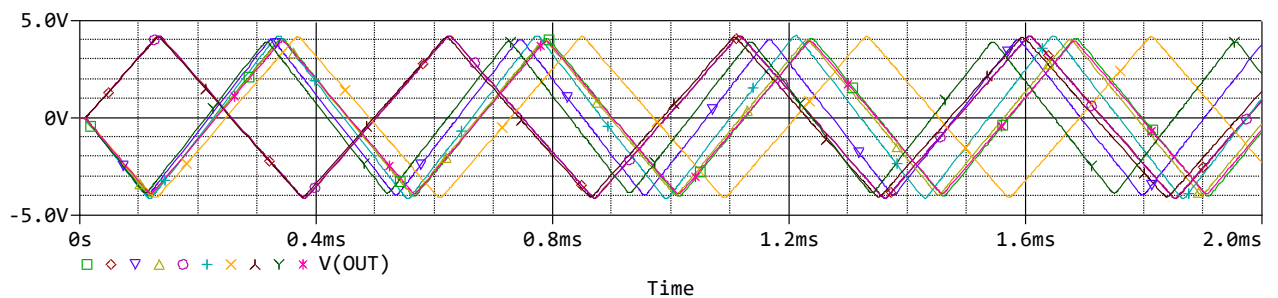

Graph 4- Monte Carlo Analysis

The results of the Monte Carlo analysis show that the maximum value of the voltage at the output that can be obtained is 4.23V, whereas the minimum value is 3.92V, and the mean value is 4.098V, which is satisfying the desired conditions.

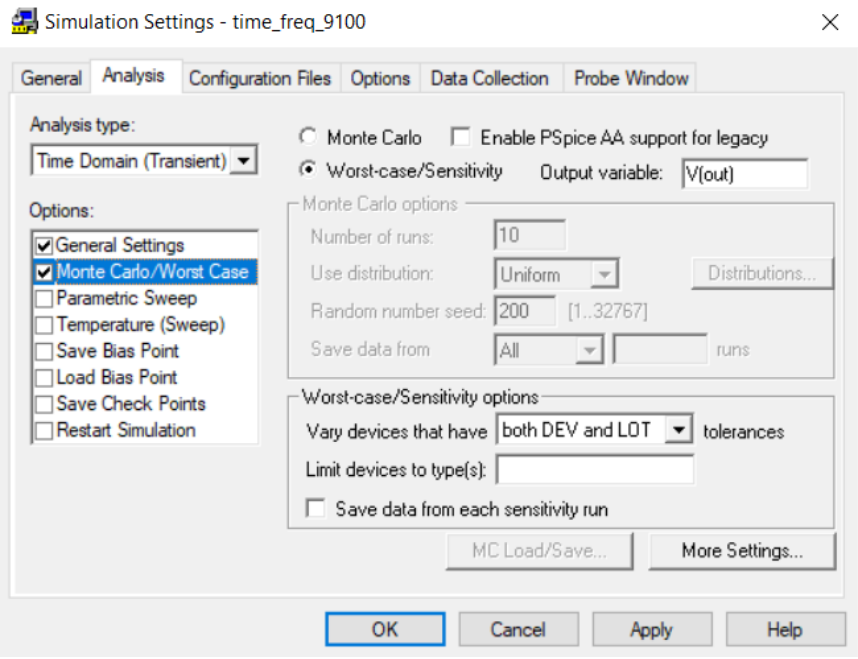Results of running a **Worst Case sensitivity analysis** on the **triangle wave** :



Simulation setting 2-Worst Case

Output file of the simulation:


```

                                WORST CASE ALL DEVICES
*****
Device      MODEL      PARAMETER  NEW VALUE
C_C4        C_C4         C          1.1      (Increased)
R_R8        R_R8         R          .999     (Decreased)
R_R3        R_R3         R          .999     (Decreased)
R_R2        R_R2         R          1.001    (Increased)
R_R14       R_R14        R          .999     (Decreased)
R_R18       R_R18        R          1.01     (Increased)
R_LOAD      R_LOAD       R          1.001    (Increased)
R_R7        R_R7         R          .95      (Decreased)
R_R15       R_R15        R          .9        (Decreased)
R_R16       R_R16        R          1.001    (Increased)
R_Rp2       R_Rp2        R          .95      (Decreased)
R_Rp3       R_Rp3        R          .95      (Decreased)
R_Rp        R_Rp         R          .99      (Decreased)
R_Rp1       R_Rp1        R          .99      (Decreased)
^
**** 06/02/21 17:25:48 ***** PSpice 17.2.0 (March 2016) ***** ID# 0 *****
** Profile: "SCHEMATIC1-time_freq_9100" [ d:\cad\signal_generator-pspicefiles\schematic1\time_freq_9100.sim ]

****      SORTED DEVIATIONS OF V(OUT)      TEMPERATURE = 27.000 DEG C

                                WORST CASE SUMMARY
*****
```

It can be seen that the most significant modifications were done regarding the capacitance, and resistors R2,R18,R16 and also at the load, although the load has a small tolerance, of 0.1%.

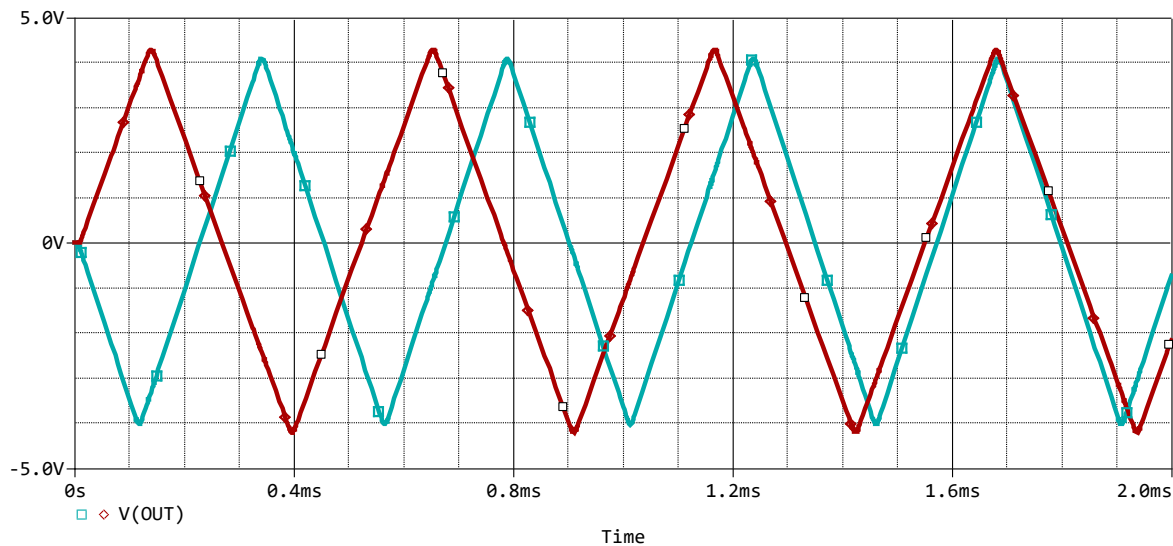


Graph 5-Worst Case analysis on the triangle wave

Results of **running worst case analysis** when v(out)= **rectangular of 4V**

WORST CASE ALL DEVICES				

Device	MODEL	PARAMETER	NEW VALUE	
C_C4	C_C4	C	.9	(Decreased)
R_R8	R_R8	R	.999	(Decreased)
R_R3	R_R3	R	.999	(Decreased)
R_R2	R_R2	R	1.001	(Increased)
R_R14	R_R14	R	1.001	(Increased)
R_R18	R_R18	R	1.01	(Increased)
R_LOAD	R_LOAD	R	.999	(Decreased)
R_R7	R_R7	R	1.05	(Increased)
R_R15	R_R15	R	.9	(Decreased)
R_R16	R_R16	R	.999	(Decreased)
R_Rp2	R_Rp2	R	1.05	(Increased)
R_Rp3	R_Rp3	R	.95	(Decreased)
R_Rp	R_Rp	R	.99	(Decreased)
R_Rp1	R_Rp1	R	.99	(Decreased)

**** 06/02/21 17:31:58 ***** PSpice 17.2.0 (March 2016) ***** ID# 0 *****				
** Profile: "SCHEMATIC1-time_freq_9100" [d:\cad\signal_generator-pspicefi				
**** SORTED DEVIATIONS OF V(OUT) TEMPERATURE = 27.000 DEG C				

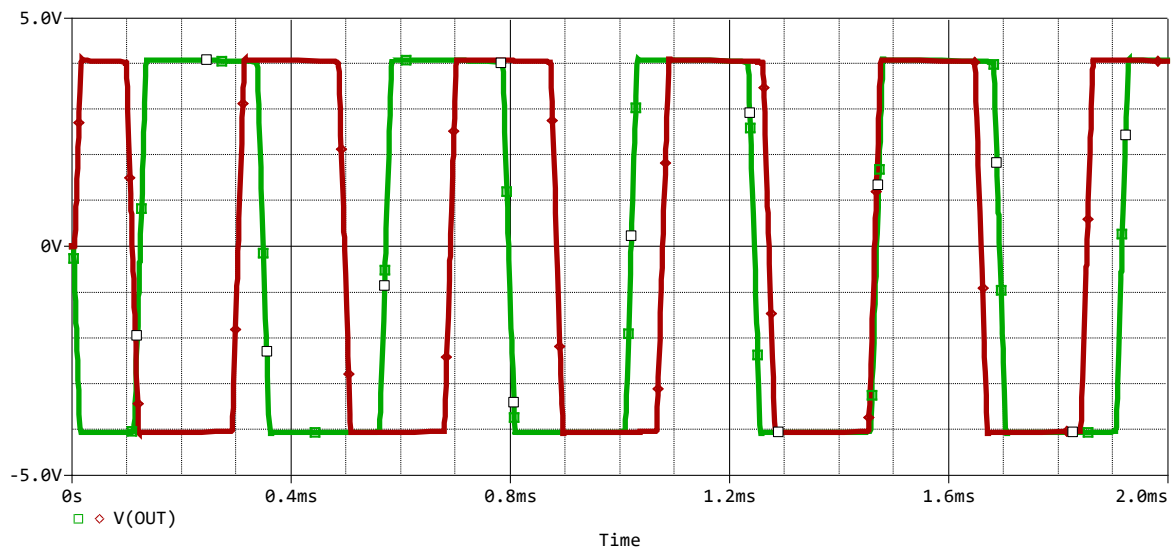

Graph 6-Worst Case of rectangular of 4V

With green is the output resulted by using the nominal values, and with red is the output considered in the worst case possible.

Results of **running worst case analysis** when v(out)= **rectangular of 7V**

WORST CASE ALL DEVICES


Device	MODEL	PARAMETER	NEW VALUE	
C_C4	C_C4	C	1.1	(Increased)
R_R8	R_R8	R	1.001	(Increased)
R_R3	R_R3	R	1.001	(Increased)
R_R2	R_R2	R	.999	(Decreased)
R_R14	R_R14	R	1.001	(Increased)
R_R18	R_R18	R	.99	(Decreased)
R_LOAD	R_LOAD	R	.999	(Decreased)
R_R7	R_R7	R	.95	(Decreased)
R_R15	R_R15	R	.9	(Decreased)
R_R16	R_R16	R	.999	(Decreased)
R_Rp2	R_Rp2	R	.95	(Decreased)
R_Rp3	R_Rp3	R	1.05	(Increased)
R_Rp	R_Rp	R	1.01	(Increased)
R_Rp1	R_Rp1	R	.99	(Decreased)



**** 06/02/21 17:29:35 ***** PSpice 17.2.0 (March 2016) ***** ID# 0 *****

** Profile: "SCHEMATIC1-time_freq_9100" [d:\cad\signal_generator-pspicef:

**** SORTED DEVIATIONS OF V(OUT) TEMPERATURE = 27.000 DEG C

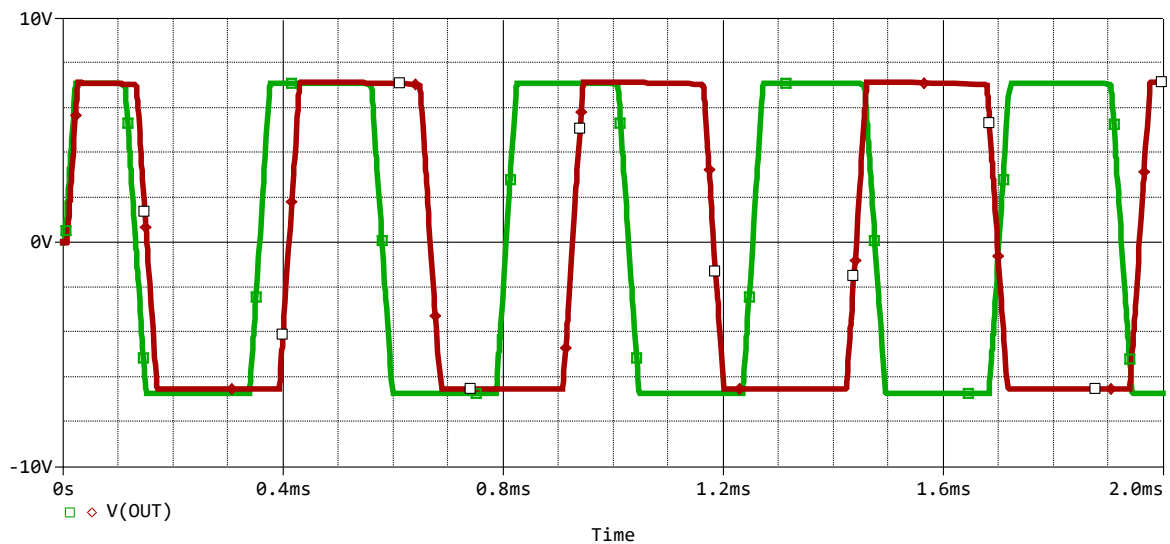


Graph 7-Worst Case- Rectangular of 7V


With green is the output resulted by using the nominal values, and with red is the output considered in the worst case possible. In this case, it deviates to much from the nominal value, in comparison when a signal of 4V needs to be obtained.

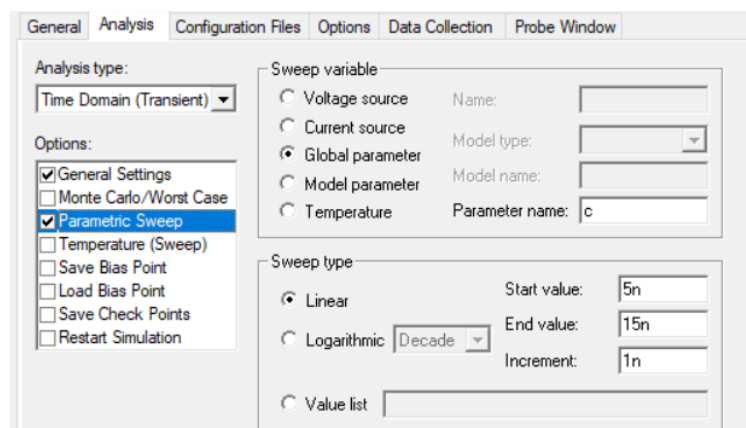c. Parametric Analysis

- Below is the variation of the output signal when it is swept over the **capacitance** :




Simulation setting 3-Capacitance sweeping

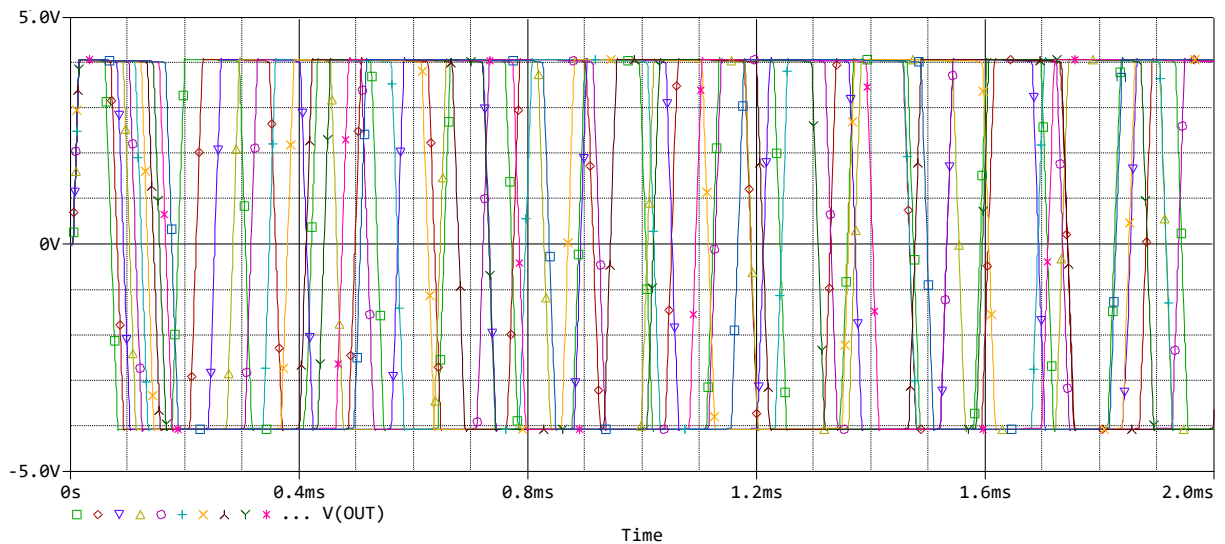


Graph 8-Output swept over the capacitance

It can be seen that the signals are not perfect rectangles, but they reach $\pm 4V$.

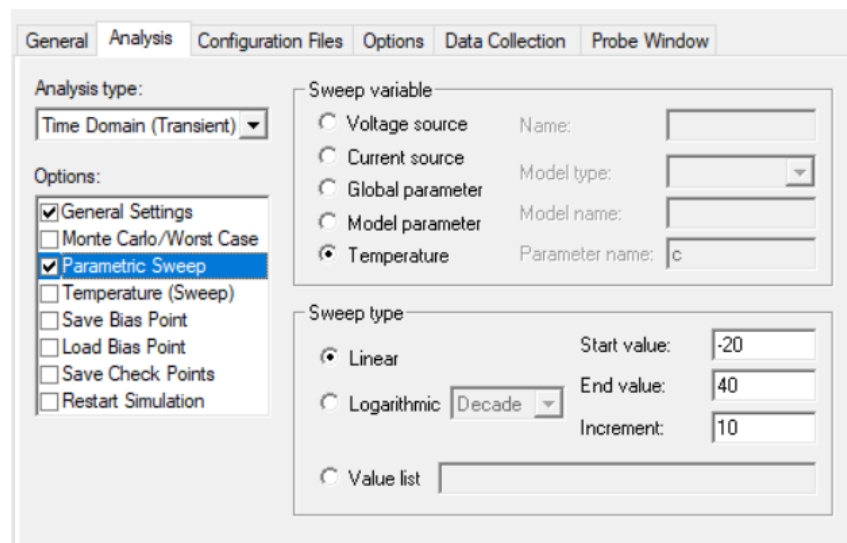➤ Below is the variation of the output signal when it is swept over the temperature:




Simulation setting 4-Temperature sweeping

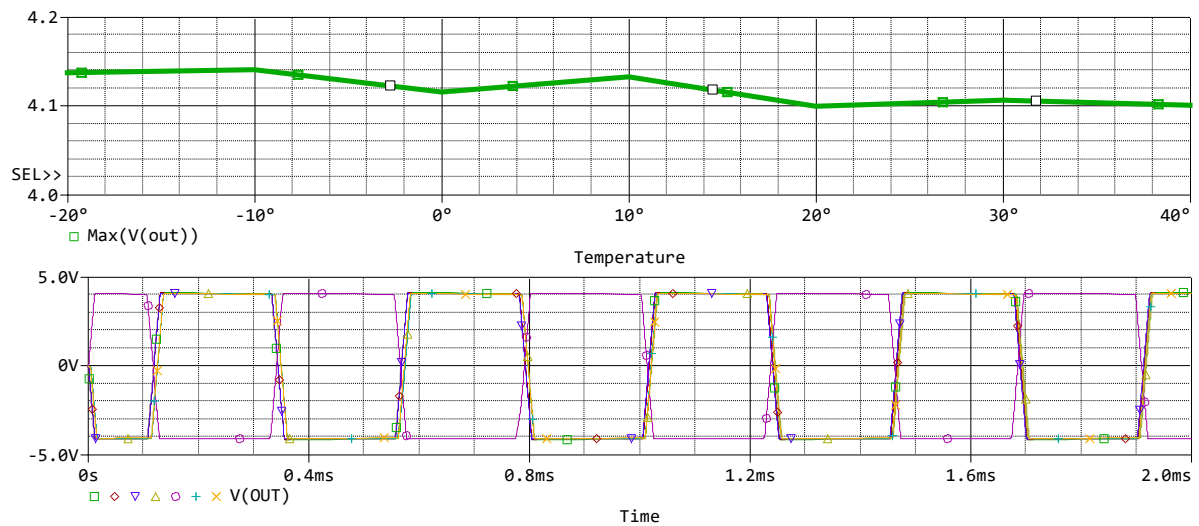

Graph 9-Output swept over the temperature

It can be seen that the output varies between **4.14V** at $T=-20^\circ$ and **4.1V** at $T=40^\circ$, which is not such a great deviation, so the circuit behaves good in standard temperature conditions.

Also, to prove the functioning of the power amplifier of the circuit I established another transient analysis in which I compared the current at the output of the UA741 OpAmp with the current through the load .

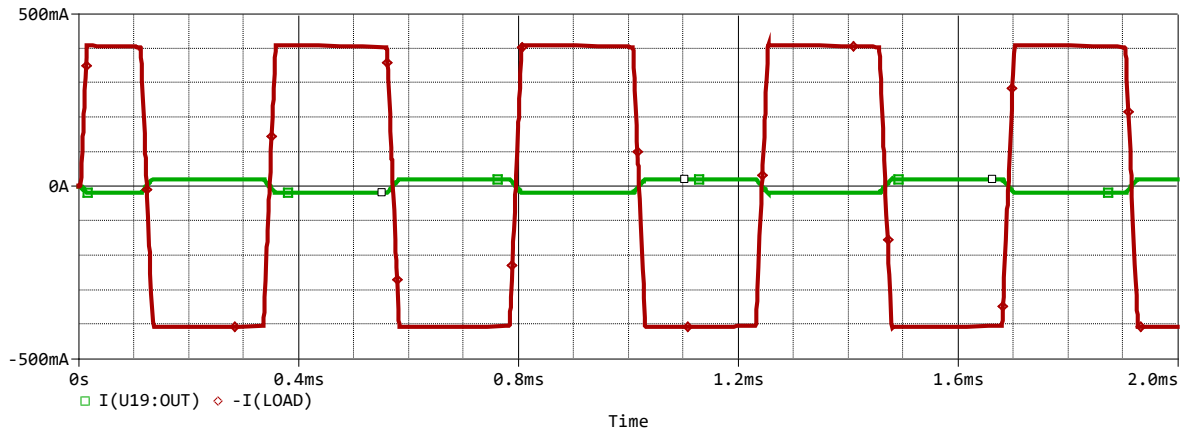

Graph 10-Currents through the load and the output at the OpAmp

<input checked="" type="checkbox"/>	Max(I(LOAD))	410.32528m
<input checked="" type="checkbox"/>	Max(I(U19:OUT))	20.80018m

As expected, the UA741 can only provide 20mA, while the load needs around 400mA to function properly.

5 Conclusions

As an overview, the triangle wave manages to achieve $\pm 4V$ as expected, and the waveform is a perfect triangle at the frequency of 2237Hz. The range of desired frequencies was 2400Hz and 9100Hz, but this signal generator can only output waves of a maximum of 8130Hz, due to inappropriate resistance biasing.

The rectangle wave behaves best when it has an amplitude of 4V. The wave has a good shape and the amplitude doesn't deviates too much from the required one. It can achieve as the triangle, frequencies between 2237Hz and 8130Hz. When the potentiometer is set to provide an amplitude of 7V, the signal looks more like a trapeze, probably it is due to the time constant. When the frequency is 8130Hz, the rectangular signal has a greatly deviated shape at both 4V and 7V.

Overall, I can say that the performance of this signal generator is acceptable. Although the frequency range is not the one required, and the waveforms may vary, it still reaches the amplitudes for which it was designed in standard conditions.

Bibliography

- [1] Thomas L. Floyd, Electronic Devices Conventional Current Version. International Edition Seventh Edition, 2005.
- [2] (2021) <https://www.electronics-tutorials.ws/opamp/op-amp-multivibrator.html>
- [3] (2021) https://www.electronics-tutorials.ws/opamp/opamp_6.html
- [4] (2021) <http://www.learningaboutelectronics.com/Articles/Function-generator-circuit.php>
- [5] (2021) Fundamental Electronic Circuits course, Prof. Gabriel Oltean http://www.bel.utcluj.ro/dce/didactic/fec/20_nonsinusoidal_oscillators.pdf
- [6] (2021) <https://www.allaboutcircuits.com/video-tutorials/op-amp-applications-voltage-follower/>
- [7] (2021) <https://www.allaboutcircuits.com/technical-articles/how-to-buffer-an-op-amp-output-for-higher-current-part-1/>
- [8] (2021) <https://www.eeeguide.com/triangular-wave-generator-using-op-amp/>
- [9](2021) http://www.bel.utcluj.ro/dce/didactic/fec/14_power_amplifier_class_B_AB.pdf
- [10](2021) <https://ukdiss.com/examples/class-ab-audio-amplifier.php>